HOME PLOTS APPS EDITOR PUBLISH VIEW

New Open Save Print Compare Go To Find Bookmark Copilot Refactor Profiler Code Issues Debugger Generate Test Find Tests Run Section Section Break Run and Advance Run to End Run Step

FILE NAVIGATE CODE ANALYZE TEST

C: › Users › HP › Downloads ›

Files

Name

_Getintopc.com_Optiwave_...
_temp_matlab_R2026a_Win...
_temp_matlab_R2026b_Win...
Camera Roll
Documents
ES
lol
OptiSystem-23.0.0-evaluatio...
Saveetha_Browser
Vivado_Lab_Lin_2024.1_052...
_Getintopc.com_Altium_Desi...
_Getintopc.com_Optiwave_...
00BCCGYKAAAAYD4D0J29...

Workspace

Name	Value	Size
I1_oc	2	1×1
I2_oc	4	1×1
V1_oc	12	1×1
V1_oc2	8	1×1
V2_oc	6	1×1
V2_oc2	16	1×1
Z	[6,2;3,4]	2×2
Z11	6	1×1
Z12	2	1×1
Z21	3	1×1
Z22	4	1×1

Editor

ECA56-EXP-1.m × EXP1.m ×

C:\Users\HP\Downloads\EXP1.m

```
1
2       clc;
3       clear;
4       close all;
5
6       % EX NO: 1.1
7       % Determination of Low-Frequency Network Parameters
8       % of a Two-Port Network using MATLAB
9
10      % Given Measurements
11
12      % Case 1: I2 = 0 (Output Port Open Circuited)
13      V1_oc = 12;   % Input Voltage (V)
14      V2_oc = 6;    % Output Voltage (V)
15      I1_oc = 2;    % Input Current (A)
16
17      % Case 2: I1 = 0 (Input Port Open-Circuited)
18      V1_oc2 = 8;   % Input Voltage (V)
19      V2_oc2 = 16;  % Output Voltage (V)
20      I2_oc = 4;    % Output Current (A)
21
22      % Calculation of Z-Parameters
23
24      Z11 = V1_oc / I1_oc;
```

Command Window

New to MATLAB? See resources for Getting Started

```
Z22 = 4.00 Ohms
Z-Parameter Matrix =
     6     2
     3     4

>>
```


Figures

FIGURE FORMAT TOOLS LAYOUT

Save As Copy Figure Print Show Code Title Subtitle X-Label Y-Label Legend Colorbar Grid

FILE LABELS AND ANNOTATIONS

Figure 1 ×

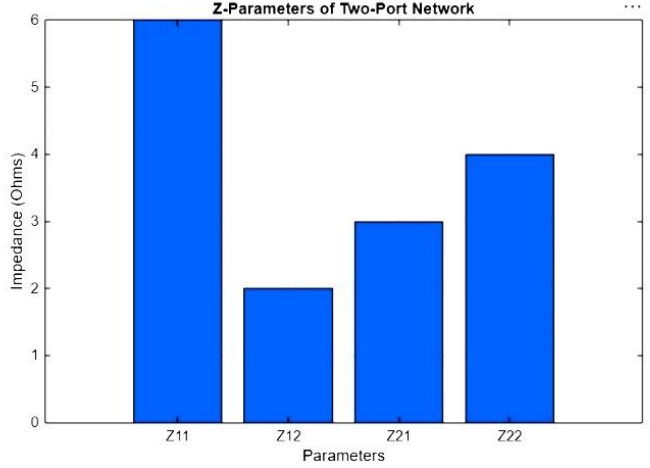

Ask Copilot

Validate generated output before use.